

H.T No:

--	--	--	--	--	--	--	--	--	--

R22



CMR COLLEGE OF ENGINEERING & TECHNOLOGY
(UGC AUTONOMOUS)

Examination : B.Tech IV Sem Supplementary Examinations January-2025
Course Name : Analog & Digital Communications
Course Code : A404304
Branch : Electronics & Communication Engineering
Date & Session : 07-01-2025 AN **Duration: 3 hours** **Max. Marks: 60**

(Note: Assume suitable data if necessary)

PART-A

Answer all TEN questions
Each question carries ONE mark.

10x1=10M

1. What is the need for modulation? 1 M
2. Draw the Phasor representation of an AM Wave? 1 M
3. Define frequency deviation? 1 M
4. What are the salient features of Phase modulation? 1 M
5. Define selectivity of AM receiver? 1 M
6. Identify the purpose of limiter in an FM receiver? 1 M
7. Discuss the main features of Delta Modulation? 1 M
8. How can the Quantization error can be reduced? 1 M
9. Define ISI? 1 M
10. How is eye pattern obtained on the CRO? 1 M

PART-B

Answer the following. Each question carries TEN Marks.

5x10=50M

- 11.A). The carrier` frequency for AM modulator is 500khz.The maximum modulating signal is 1kHz. Find i) The upper and lower sideband ii) the bandwidth iii) If the modulating signal frequency is 1500kHz, Find the lower and upper sideband frequencies iv) Draw the output frequency spectrum for $f_m=1\text{kHz}$. 10M

OR

11. B). With the help of block diagram explain the production of SSB SC and compare with the VSB SC. 10M
12. A). Demonstrate the detection of FM using Phase Locked Loop (PLL). 10M

OR

12. B). With a neat block diagram explain the Armstrong method of FM generation. 10M
13. A). Implement the following: 10M
- i) List the Advantages and disadvantages of TRF receiver?
 - ii) Discuss in detail about pre-emphasis and de-emphasis in FM.

OR

13. B). Draw the block diagram of superheterodyne radio receiver and explain the function of each block. 10M

(P.T.O.)

14. A). Explain the Operation of DPCM techniques. List the advantages and disadvantages of it. 10M

OR

14. B). Explain Delta modulation with block diagram and discuss different types of noise effects in Delta modulation. 10M

15. A). What are different digital modulation techniques available? Compare them with regard to the probability error. 10M

OR

15. B). Explain generation and detection of coherent binary PSK and differential phase shift keying signals. 10M

H.T No:

--	--	--	--	--	--	--	--	--	--

R22



CMR COLLEGE OF ENGINEERING & TECHNOLOGY
(UGC AUTONOMOUS)

Examination : B.Tech IV Sem Supplementary Examinations January-2025
Course Name : Electromagnetic fields and Transmission Lines
Course Code : A404306
Branch : Electronics & Communication Engineering
Date & Session : 09-01-2025 AN **Duration: 3 hours** **Max. Marks: 60**

(Note: Assume suitable data if necessary)

PART-A

Answer all TEN questions

Each question carries ONE mark.

10x1=10M

1. What is the unit of volume charge density? 1 M
2. What is the Electric field Intensity due to surface charge density. 1 M
3. What is the Units of Magnetic Flux Density? 1 M
4. Relation between direction of magnetic force and direction of velocity of charged particle. 1 M
5. Define Faraday's law. 1 M
6. What is first Maxwell equation? 1 M
7. What is the intrinsic impedance in free space? 1 M
8. Write the equation for Phase constant in free space. 1 M
9. What is lossless line 1 M
10. Obtain the relation for Reflection co-efficient in terms of Z_L and Z_0 . 1 M

PART-B

Answer the following. Each question carries TEN Marks.

5x10=50M

- 11.A). i) State and explain Coulomb's law using vector form of Coulomb's force expression. 5M
ii) Find the force on a charge of -100mC located at P (2, 0, 5) in free space due to another charge 300 μ C located at Q (1, 2, 3). 5M

OR

11. B). Define and distinguish between the terms electric field, electric displacement, electric flux density and derive mathematical relations. 10M

12. A). What is amperes force law and derive force between two current elements. 10M

OR

12. B). Develop an expression for the magnetic field intensity using Biot savart's law. 10M

13. A). Derive the boundary conditions for the tangential components of Electrostatic fields at the boundary between two perfect dielectrics. 10M

OR

13. B). i) Define maxwells equations in word statements and give differential & integral form. 5M
ii) Derive expression for Poynting theorem. 5M

(P.T.O.)

14. A). Derive the relation $E/H = \eta$ for uniform plane wave. 10M

OR

14. B). Derive expression for Reflection coefficient of an EM wave when it is incident obliquely on a dielectric. 10M

15. A). i) Derive the expression for single stub matching. 7M

ii) Write a detailed notes on Smith chart and its applications. 3M

OR

15. B). Derive transmission line equations. 10M

H.T No:

--	--	--	--	--	--	--	--	--	--

R22



CMR COLLEGE OF ENGINEERING & TECHNOLOGY
(UGC AUTONOMOUS)

Examination : B.Tech IV Sem Supplementary Examinations January-2025
Course Name : Linear and Digital IC Applications
Course Code : A404307
Branch : Electronics & Communication Engineering
Date & Session : 10-01-2025 FN **Duration: 3 hours** **Max. Marks: 60**

(Note: Assume suitable data if necessary)

PART-A

Answer all TEN questions

Each question carries ONE mark.

10x1=10M

1. Define CMRR of op-amp. 1 M
2. Define input offset voltage. 1 M
3. Define lock range in PLL. 1 M
4. Why active filters are preferred. 1 M
5. Name the different DAC techniques. 1 M
6. Define Resolution of ADC. 1 M
7. Write the examples of Combinational Circuits. 1 M
8. Define Binary Comparator. 1 M
9. Classify types of ROMs. 1 M
10. Draw the Excitation Table of SR. 1 M

PART-B

Answer the following. Each question carries TEN Marks.

5x10=50M

- 11.A). What is an Instrumentation amplifier? Explain the working of instrumentation amplifier with neat circuit diagram. 10M

OR

11. B). Explain the internal structure of voltage regulator IC 723. Also draw a voltage Regulator circuit using IC 723 and explain its operation. 10M

12. A). Draw the block diagram of monostable multivibrator using 555 timer and derive an expression for its pulse width. 10M

OR

12. B). Explain working of PLL using appropriate block diagram. 10M

13. A). i) With a neat diagram, explain the working principle of R-2R ladder type DAC. 5M
ii) Write the specifications of DAC. 5M

OR

13. B). Explain the operation of parallel comparator type ADC. 10M

14. A). Design 3 to 8 decoder and explain its operation. 10M

OR

14. B). Design 2 bit Magnitude Comparator. 10M

15. A). i) Design a Modulo-10 Synchronous counter using any flip flop. 5M
ii) Write the differences between synchronous and asynchronous counters. 5M

OR

15. B). Discuss in detail ROM access mechanism with the help of timing waveforms. 10M

H.T No:

--	--	--	--	--	--	--	--	--	--

R22



CMR COLLEGE OF ENGINEERING & TECHNOLOGY
(UGC AUTONOMOUS)

Examination : B.Tech IV Sem Supplementary Examinations January-2025
Course Name : Electronics Devices and Circuits
Course Code : A404203S
Branch : Electronics & Communication Engineering
Date & Session : 17-01-2025 AN **Duration: 3 hours** **Max. Marks: 60**

(Note: Assume suitable data if necessary)

PART-A

Answer all TEN questions
Each question carries ONE mark.

10x1=10M

1. What is a diode? 1 M
2. List two types of capacitance in diodes. 1 M
3. What is a half-wave rectifier? 1 M
4. Draw the clipper circuit. 1 M
5. State the function of a transistor. 1 M
6. Name the configurations of Bipolar Junction Transistor (BJT). 1 M
7. What does FET stand for? 1 M
8. Define MOSFET in simple terms. 1 M
9. What is the use of a Zener diode? 1 M
10. List one application of an LED. 1 M

PART-B

Answer the following. Each question carries TEN Marks.

5x10=50M

- 11.A). A diode has a forward voltage of 0.7V and dynamic resistance of 5Ω . Calculate the current flowing through the diode if a 5V source is applied across it. 10M

OR

11. B). Explain the VI characteristics of a diode with the help of a diagram, including both forward and reverse bias regions. 10M

12. A). Describe the working of a full-wave rectifier with a capacitor filter. 10M

OR

12. B). Explain clamping operation and types of clampers. 10M

13. A). Discuss the principle of operation of a Bipolar Junction Transistor with its types. 10M

OR

13. B). Compare common base and common collector configurations. 10M

14. A). i) Develop input and output characteristics of transistor in CC configuration. 5M
ii) Formulate the relationship between α , β and γ . 5M

OR

14. B). Build a circuit for obtaining of Drain and Transfer characteristics of an N-Channel JFET. 10M

15. A). i) Analyze the how Zener diode is used as voltage regulator? 5M
ii) Compare avalanche and Zener diode break down. 5M

OR

15. B). Explain the principle of operation of a photodiode and LED. 10M

.....

H.T No:

--	--	--	--	--	--	--	--	--	--

R22



**CMR COLLEGE OF ENGINEERING & TECHNOLOGY
(UGC AUTONOMOUS)**

Examination : B.Tech IV Sem Supplementary Examinations Jan-2025

Course Name : Electronic Circuit Analysis

Course Code : A404308

Branch : ECE

Date & Session : 25-01-2025 FN

Duration: 3 hours

Max. Marks: 60

(Note: Assume suitable data if necessary)

PART-A

Answer all TEN questions

Each question carries ONE mark.

10x1=10M

1. Compare the efficiency of Class A and Class B power amplifier 1 M
2. Why h-parameters are not used for analysis of power amplifiers 1 M
3. Define unloaded and loaded Q of tuned circuit. 1 M
4. List the advantages of tuned amplifiers 1 M
5. Calculate time period of astable mutli if $R_1=1K\Omega$, $C_1=10\mu F$ $R_2=2K\Omega$
 $C_2=20\mu F$ 1 M
6. What are different types of triggering? 1 M
7. Define slope error? 1 M
8. What are different types of time-based generators available 1 M
9. Draw the circuit diagram of monostable relaxation circuit 1 M
10. What are the advantages of synchronization circuits 1 M

PART-B

Answer any FIVE questions. One question from each unit either A or B (Compulsory)

Each question carries TEN Marks.

5x10=50M

11. A. Show that in push pull stage distortion decreases 10M
- OR
11. B. Show that the maximum efficiency of Class-A power amplifier is 50% 10M
12. A. Explain the operation of Single stage tuned amplifiers and also its resonance frequency 10M
- OR
12. B. Define Q factor. With the help of circuit diagram explain about double tuned amplifier circuit. 10M
13. A. With the help of neat sketch explain the operation of mono stable multi and derive the expression for pulse width 10M
- OR
13. B. With the help of neat sketch explain the operation of astable multi and derive the expression for time period of generated square wave 10M

(P.T.O.)

14. A. Derive the following expressions for 10M
a) Sweep speed error b) Displacement error c) Transmission error

OR

14. B. Find the component values of a bootstrap sweep generator, Given $V_{CC} = 20$ 10M
 V , $I_{C(sat)} = 3$ mA and $h_{fe}(\min) = 50$.

15. A. Why the sampling gates are called linear gates and compare unidirectional 10M
and bidirectional sampling gates.

OR

15. B. With the help of neat diagram explain the working of a six-diode gate? 10M

15. A). Write short notes on state equivalence and machine minimization.

10M

OR

15. B). What is merger table method? Explain with suitable example.

10M

13. A. The impulse response of a system is $h(t) = e^{-2t} u(t)$ and the input to the system is $x(t) = e^{-4t} [u(t) - u(t-3)]$. Determine the output response of the system using Graphical interpretation of Convolution. 10M

OR

13. B. Let the system function of an LTI System be $H(\Omega) = \frac{1}{1+j\Omega}$. determine the output response for an input $x(t) = (0.8)^t u(t)$ 10M

14. A. State and prove initial value theorem and final value theorem of Laplace Transforms. Find initial and final values of the following Laplace functions. 10M

$$(a) X(s) = \frac{s+4}{s^2+3s+5}$$

$$(b) X(s) = \frac{s^2+3s+6}{s^2+2s+3}$$

OR

14. B. Find the Z-Transform of the sequence 10M

$$x(n) = \left(\frac{1}{2}\right)^n \cos\left(\frac{\pi}{3}n\right) u(n) \text{ Also sketch the ROC and pole-zero location.}$$

15. A. Explain Flat top Sampling technique with neat circuit diagram and necessary waveforms. And also discuss the aperture effect. 10M

OR

15. B. State and prove the properties of Energy Spectral Density(ESD). And also prove that autocorrelation function and ESD will form a Fourier Transform pair. 10M
